



**MANMOHAN TECHNICAL UNIVERSITY**  
**Office of the Controller of Examinations**  
 Budhiganga-4, Morang, Province 1, Nepal

Faculty: Engineering

Exam Year: 2080 Mangsir

Year/Part: II/I

Program: Electrical and Electronics

Level: Bachelor

F.M.: 50

Subject: ELECTRIC CIRCUIT THEORY (EG503EE)

Time: 3 Hours


P.M.: 20

- ✓ Group A contains Multiple Choice Questions of 10 marks.
- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

**Group 'B'**

**Short Answer Questions (Attempt any EIGHT questions only.)**  
**(8×2=16)**

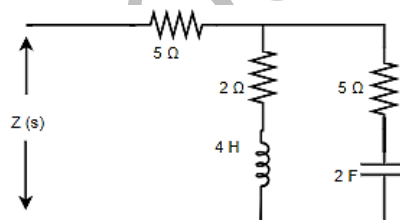1. What are the initial conditions for Inductor and Capacitors under energized and de-energized conditions?
2. Find the time constant for a series RL circuit under step response.
3. Find the partial fraction expression for:  $G(s) = \frac{2s}{s^2+3s+2}$
4. Convert the following expression in exponential form:  $\cos \beta t - j \sin \beta t$
5. Find the poles and zeros of the transfer function:  $I(s) = \frac{(s^2-3s+2)}{(s^3-5s^2)(s^2+7s+6)}$
6. How does a high pass filter circuit work?
7. Describe hybrid parameters for a two-port electrical network.
8. Write the expression for the Fourier series and its coefficients for a periodic signal.
9. Find the Driving point Impedance  $Z(s)$  for the following circuit:




**Group 'C'**


**Long Answer Questions (Attempt any SIX questions only.)**

**(6×4=24)**

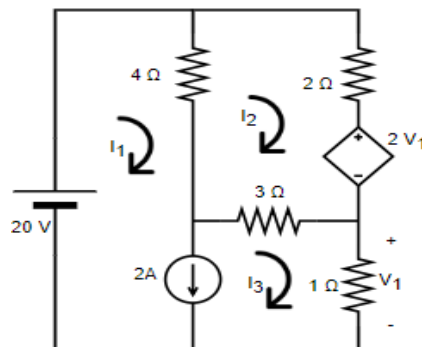
1. Find the currents  $I_1$ ,  $I_2$  and  $I_3$  using Matrix method.



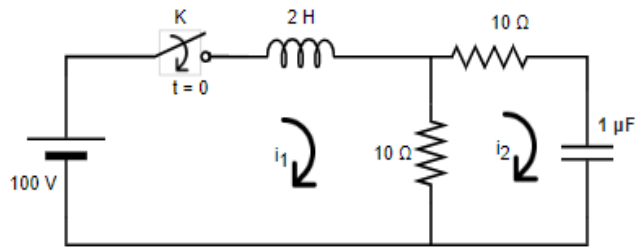
2. The switch K is initially open for a long time and it is closed at  $t=0$ . Find  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$ ,  $\frac{di_2}{dt}$  at  $t = 0^+$ .



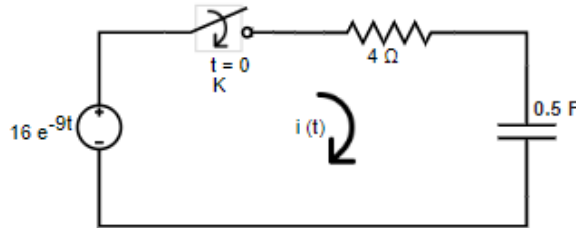3. Solve for  $i(t)$  at  $t > 0$  using Classical Method.



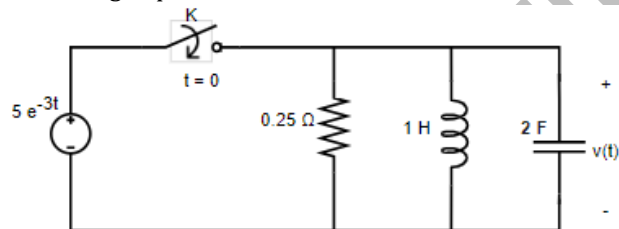
4. Solve for  $v(t)$  at  $t > 0$  using Laplace Transform Method.




5. Draw the Bode Magnitude Plot Diagram for the following network function:

$$H(s) = \frac{20(s+1)}{s(s+5)(s+15)}$$

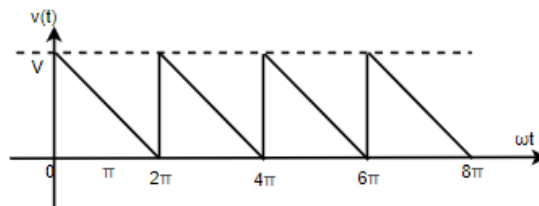6. Find the Trigonometric form of Fourier series for the following periodic waveform:



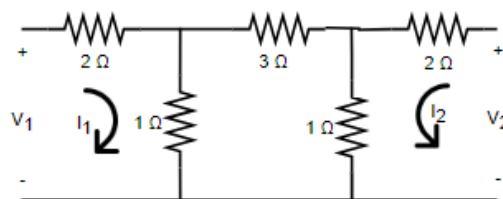7. Find the T - parameters for the two-port network shown below.



\*\*\*ALL THE BEST\*\*\*